


RPM Sensors: Tachometers

LM2917N based Frequency to Voltage Tachometer

An easy way of measuring RPM is to convert the frequency of a sensor attached to the motor into a proportional voltage. The LM2917N Frequency to Voltage Converter is designed exactly for that job. The IC comes in 2 versions, 8 pin (LM2917N-8) and 14 pin (LM2917N) versions. Both have a voltage regulator built in, so if no other chips are required, you don't need a 7805.

The minimal circuit shown first on this page gives an output of about 1 volt per 66Hz input. The input must be AC and not a pulsed DC input. This circuit is based on the 8 pin version.

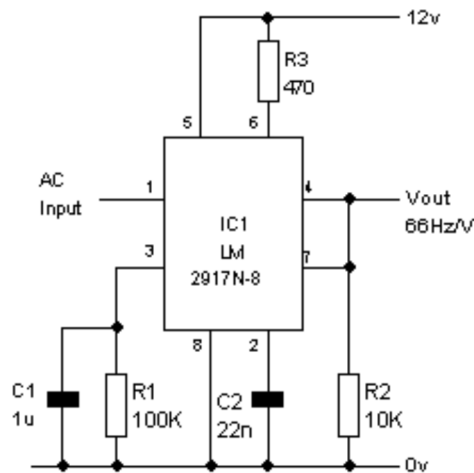$V_{out} = V_{cc} \times F_{in} \times R1 \times C2$: where F_{in} =input frequency in hertz, $R1$ =resistance connected to pin 3, $C2$ =capacitance connected to pin 2, and V_{cc} is not 12, but instead 7.5 volts (from the on-board regulator).



In the more practical circuit shown next, the input is conditioned by $R1 - R3$ and $C1$ to convert a simple switch closure (such as the points in an automotive ignition) into an AC signal suitable for the 2917. The output is smoothed by $R6/C4$ and fed into a LM3914 based bar graph display driver. Two pots adjust the scale and range of the display. This circuit is based on the 14 pin version.

